

Extended MIPS Processor

Marty Townley and Adam Ness

ECE425

Spring 2017

Introduction

Throughout the course of the semester, we have been working with the Harvey Mudd MIPS processor. For this project, we added additional functionality to this processor by altering specific parts of the given controller and datapath. Through this work we were able to add XOR and NOR instruction ability, as well as several shift operations, namely SLL, SRL, and SRA.

System Description

Features Added

Extended ALU

In order to execute all bitwise operations in the MIPS instruction set, the original ALU had to be extended to handle XOR and NOR operations. This was done by removing several logic gates prior to the Full Adder, and replacing them with a 4-1 multiplexer. This expanded the number of ALU control signals to seven. These changes were made on a slice level, then using Magic “array” commands to form the eight ALU bitslices into the full ALU used within the MIPS datapath. The changes to the ALU control signals then required a rework of the ALU decoder, which was later included in the Control Unit (discussed in Section IV).

Funnel Shifter

Similar to the extension of the ALU, the existing datapath required additional hardware in order to handle shift operations. To facilitate this functionality, we added an Array Funnel Shifter below the existing datapath. The shifter designed allows for three additional instructions to be performed, Shift Left Logical (SLL), Shift Right Logical (SRL), as well as Shift Right Arithmetic (SRA). This new hardware required additional alterations to the Extended ALU, namely replacing the 3-1 “result” multiplexer, with a 4-1 multiplexer. This allowed the outputs of the shifter to be propagated through the remainder of the datapath as required.

Operation of ALU

Operation of the extended ALU was done in multiple stages. Simulation in IRSIM was done after the addition of the XOR and NOR commands, as well as after the replacement of the 3-1 multiplexer for the 4-1 multiplexer required by the Funnel Shifter. The original ALU was removed from the datapath, and replaced with our extended ALU, which was slightly wider, due to the changed multiplexer. Functionality was again verified once the finished ALU was placed within the MIPS datapath. The results of these tests may be found in the Extended ALU section of the Simulation Plots.

Operation of Funnel Shifter

The Funnel Shifter was exhaustively simulated using IRSIM as a standalone cell (sll, slr, sra operations). Placing the shifter below the datapath allowed us to maintain the 3000 lambda width requirement, however, this caused difficulties due to the necessity of running the control signals up through the datapath. It was simulated again once placed within the datapath, alongside the extended ALU. The results of these tests may be found in the Funnel Shifter section of the Simulation Plots.

Operation of Control Unit

The Control Unit used was generated from the controller.sv module that included the new ALU control signals for the extended ALU. The aspect ratio and control signals had to be manipulated so that the controller would fit above the datapath, with signals routed down to facilitate ease of wiring to the datapath. The clock of the controller was tied to ph1 of the datapath. Correct operation of the Control Unit was confirmed using IRSIM, and executing add, sra, lb, sq, beq, and j. The results of these tests may be found in the Control Unit section of the Simulation Plots.

Operation of Overall Chip

The complete chip was simulated in IRSIM as well. The memfile.dat, which includes a MIPS program represented by eight 32-bit hexadecimal numbers was ran through the chip, as shown below:

.data:00000000	80 02 00 44	lb	v0,68(zero)	v0=5
.data:00000004	80 07 00 40	lb	a3,64(zero)	a3=3
.data:00000008	80 e3 00 45	lb	v1,69(a3)	v1=c
.data:0000000c	00 e2 20 25	or	a0,a3,v0	a0=7
.data:00000010	00 64 28 24	and	a1,v1,a0	a1=0100, 4
.data:00000014	00 a4 28 20	add	a1,a1,a0	a1=1011, 11
.data:00000018	10 a7 00 08	beq	a1,a3,0x0000003c	branch if a1=a3, doesnt
.data:0000001c	00 64 30 2a	slt	a2,v1,a0	a2 = v1 < a0 ? 0
.data:00000020	10 c0 00 01	beqz	a2,0x00000028	not equal
.data:00000024	80 05 00 00	lb	a1,0(zero)	a1=68 (44h)
.data:00000028	00 e2 30 2a	slt	a2,a3,v0	a2= a3 < v0 ? 1
.data:0000002c	00 c5 38 20	add	a3,a2,a1	a3=a2+a1 = 1+68, 45h
.data:00000030	00 e2 38 22	sub	a3,a3,v0	a3=a3-v0=64, 40h
.data:00000034	08 00 00 0f	j	0x0000003c	jump to address 0x3c
.data:00000038	80 07 00 00	lb	a3,0(zero)	a3=44h
.data:0000003c	a0 47 00 47	sb	a3,71(v0)	stores a3 into 4c
.data:00000040	00 00 00 03	sra	zero,zero,0x0	
.data:00000044	00 00 00 05	0x5		
.data:00000048	00 00 00 0c	syscall		

The program in its entirety was not able to simulate successfully, however, we believe that we traced the issue back to a flip-flop within the datapath. The data register prior to the Register File did not correctly handle the bits fed to the 2-1 multiplexer on the write data port. The results of these tests may be found in the Overall Chip section of the Simulation Plots.

Conclusion

In summary, we came close to producing a functioning 8-bit MIPS processor. The alterations we made to add XOR, NOR, as well as, SLL, SRL, and SRA instruction ability were verified through individual simulation of the respective parts. The extended ALU, Array Funnel Shifter, and Control Unit were all simulated as standalone cells, then once again after placed within the Pad Frame. The final layout was checked for design errors, then simulated again using the memfile.dat MIPS program outlined above.

Simulation Plots

Extended ALU

The following ALU tests were done after standalone testing. The waveforms below correspond to the specified instruction type, within the datapath.

AND:

op	9									
a	00101101							00101110		
b	00000010	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100
k	000									
result	00000000	00000100	00001000	00000000	00100000	00000000		00000010	00000100	00001000

OR:

op	57										
a	00110010							00110011			
b	00000010	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100	00001000
k	000										
result	00110010	00110110	00111010	00110010		01110010	10110010	00110011		00110111	00111011

NOR:

op	65										
a	11000011							11000100			
b		00000010	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100
k	000										
result	00111100	00111000	00110100	00101100	00011100	00111100		00111010	00111001	00111011	

XOR:

op	49									
a	01100101					01100110				
b	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100	00010000
k	000									
result	01100001	01101101	01110101	01000101	00100101	11100101	01100111	01100100	01100010	01101110

ADD:

op	40										
a	00010010						00010011				
b	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100	00001000	00010000
k	000										
result	00010110	00011010	00100010	00110010	01010010	10010010	00010100	00010101	00010111	00011011	

SUB:

op	84										
a	01001000					01001001					
b	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100	00001000	00010000	00100000
k	000										
result	01000000	00111000	00101000	00001000	11001000	01001000	01000111	01000101	01000001	00111001	00101001

SLT:

op	86									
a	01100000					01100001				
b	00000100	00001000	00010000	00100000	01000000	10000000	00000001	00000010	00000100	00001000
k	000									
result	00000000				00000001	00000000				

Funnel Shifter

Similar to the tests of the extended ALU shown above, the following shifter tests were of the shifter within the datapath. Standalone tests were done prior to integration as well, and the .cmd TCL file is included in the .tar file.

SLL:

op	3										
a	11111111										
b	01001011				01001100						
k	101	110	111	000	001	010	011	100	101	110	111
result	01100000	11000000	10000000	01001100	10011000	00110000	01100000	11000000	10000000	00000000	

SRL:


op	11										
a	11111111										
b	00110101							00110110			
k	001	010	011	100	101	110	111	000	001	010	011
result	00011010	00001101	00000110	00000011	00000001	00000000		00110110	00011011	00001101	00000110

SRA:


op	15										
a	11111111										
b	01010110								01010111		
k	000	001	010	011	100	101	110	111	000	001	010
result	01010110	00101011	00010101	00001010	00000101	00000010	00000001	00000000	01010111	00101011	

Control Unit


R-Type:

 


LB, SB:

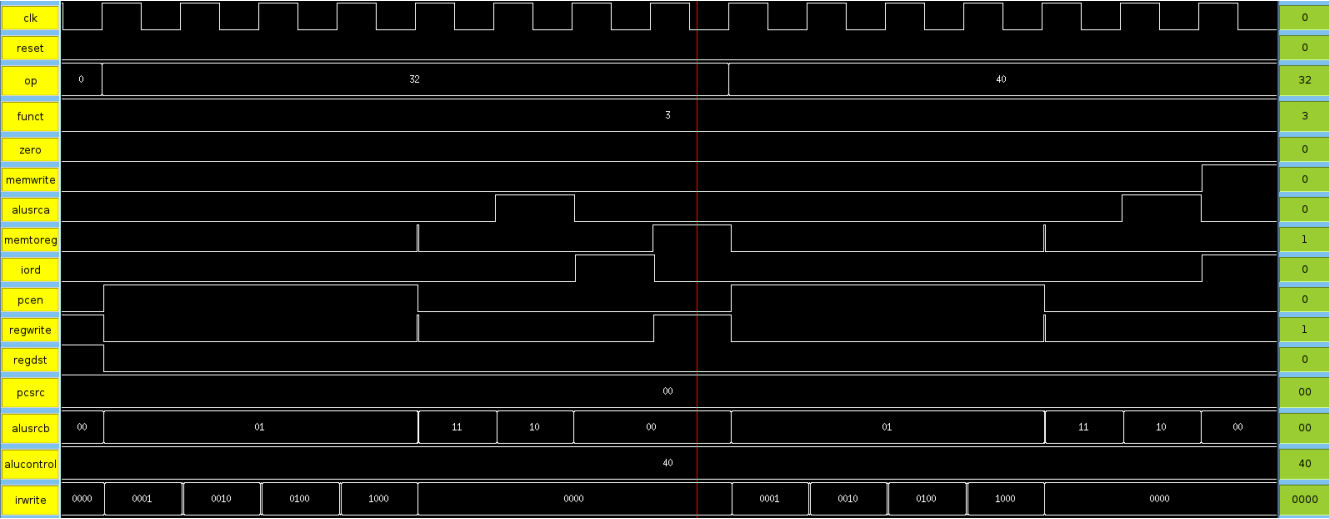


BEQ, J:

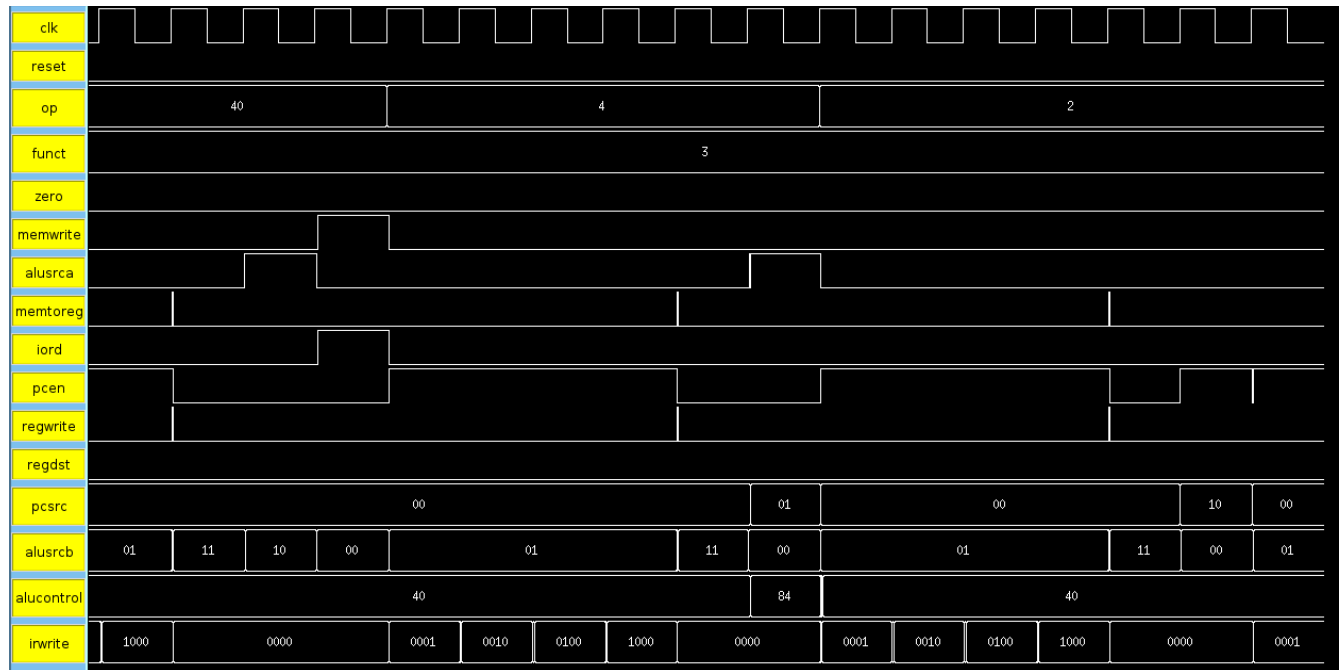

Overall Chip

 


Chip Floorplan

 


Note: Shifter shown includes source gen. + decoder logic
Dimensions listed in lambda

Layout Plots


Extended ALU

 


Funnel Shifter

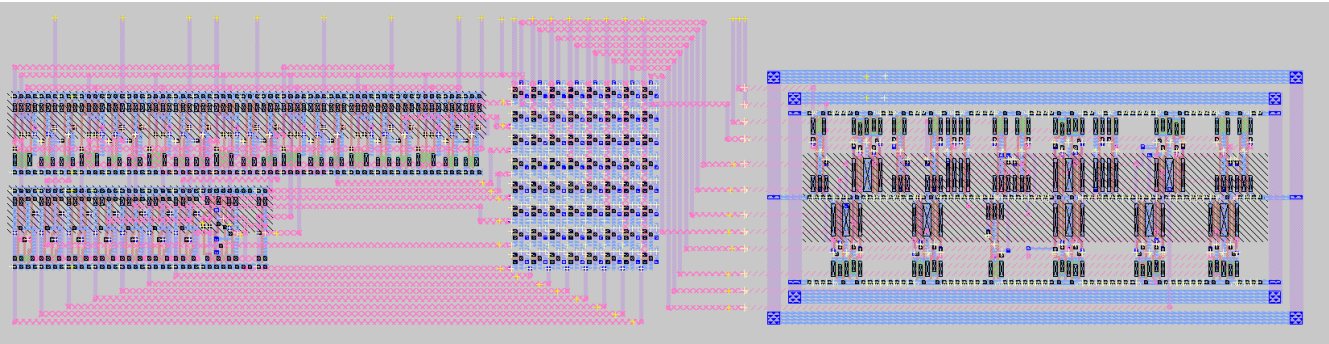

Control Unit

 

Core Cell

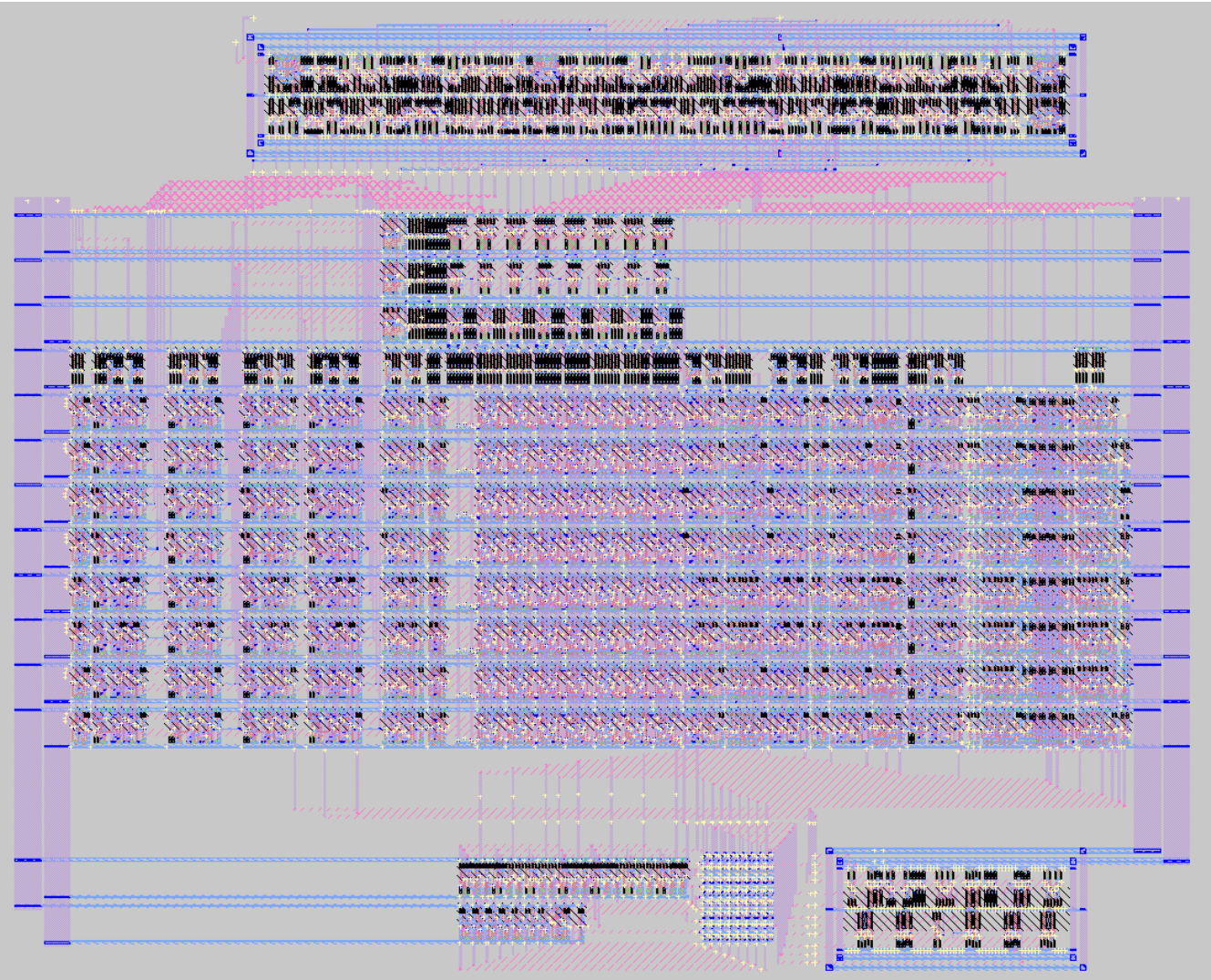

Overall Chip

